Generated from docs/ac30_schematics.jpg [CMTPC AC-30 Cassette Tape Switching Schematic].
Split into 4 sheets: docs/ac30_schematics.svg + docs/ac30_schematics-1.svg … -3.svg. Each block is wired: net labels join the blocks and sheets (identical labels are connected).
Transcription notes / assumptions:
- Pin numbers are assigned left-to-right, top-to-bottom to the real pinouts: IC7D drawn 8=+9 (VDD) 9=+10; IC12C drawn inputs 7,8 (with) 9,10;
- NJ03 NH (pin 5) and NJ1 (pin 7) are not shown on the drawing: tied to GND.
- IC15 (1488) supply pins are not shown: taken as +15V / -15V.
- IC12 (1489) supply pins are not shown: taken as +15V / -15V from the power supply (sheet 3).
- CONTROL INVERT drawn as NH2 pull-up; it is also brought out on J6.
- J6 is the 10-pin control header (+9V, GND, CONTROL INVERT, LED_REC, LED_READ).
- The front panel is wired to the rear of PJ 1/4 through-hole pads instead of the artwork's RCA sockets (switches, LEDs, pots, and the MIC/LINE 3.5 mm jacks).
- J22 (AR socket, "AUDIO_IN, EAR_A/B") is the board-edge jack that the artwork's AUDIO_IN, EAR_A/B, and EAR sockets all connect to.
- MIC/LINE switches (S2A/S2B) are ganged and work externally: J23/J24 are the mixer jacks.
- Trimmer R38 (DELAY, next to IC10 on the artwork) is not on any schematic: it is listed.
- Fuse F1 (2A) is not shown.
- The artwork's J2 pins (1,14,15 [18 INC A/B] are gone; the power supply is external.

SMT variant (kicad-smt/MCRD_SMT): every on-board part is surface mount except the Molex KK-396 power header J1 and the 3.5 mm jacks J23/J24. Diodes are SOD-123 (1N4148W, BZT52C4V7); SOD-123 diodes (1N4148W, BZT52C4V7); SOT-23 transistors (MMBT5088 for 2N3222, MMBT5087); SOT-23 Tantalum EIA-3216 (2A, 25 V): 6.3x7.7 mm aluminium C16, Bourns 3314G trimmer R18, 5206 LED DIN. RLY1/RLY2 are Omron G6K-2F-Y 5 V DPDT signal relays (the artwork's "RELAY" symbol); check the coil polarity mark (pin 1 to RELAY_+).


Mod/Demod & power input

File: AC30_SMT_modademod_powerAlead.sch

Power supply (external)

File: AC30_SMT_power_supply.kicad_sch


Front panel switches, LEDs and jacks

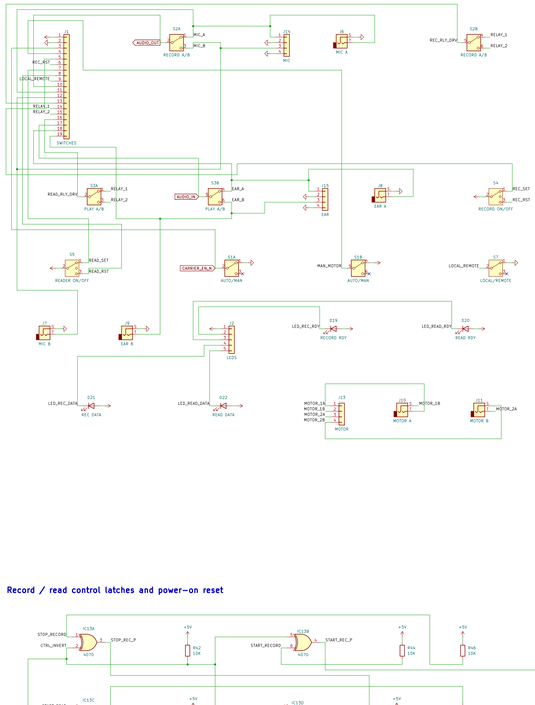


Board connectors (pin positions per original artwork)



RS-232 receivers / drivers, clock clamps

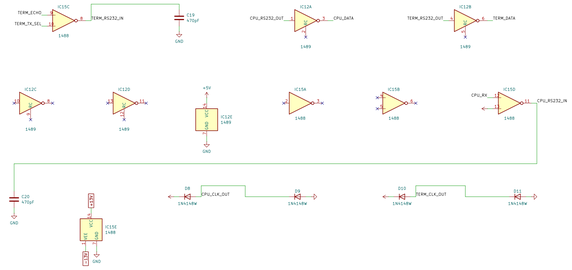

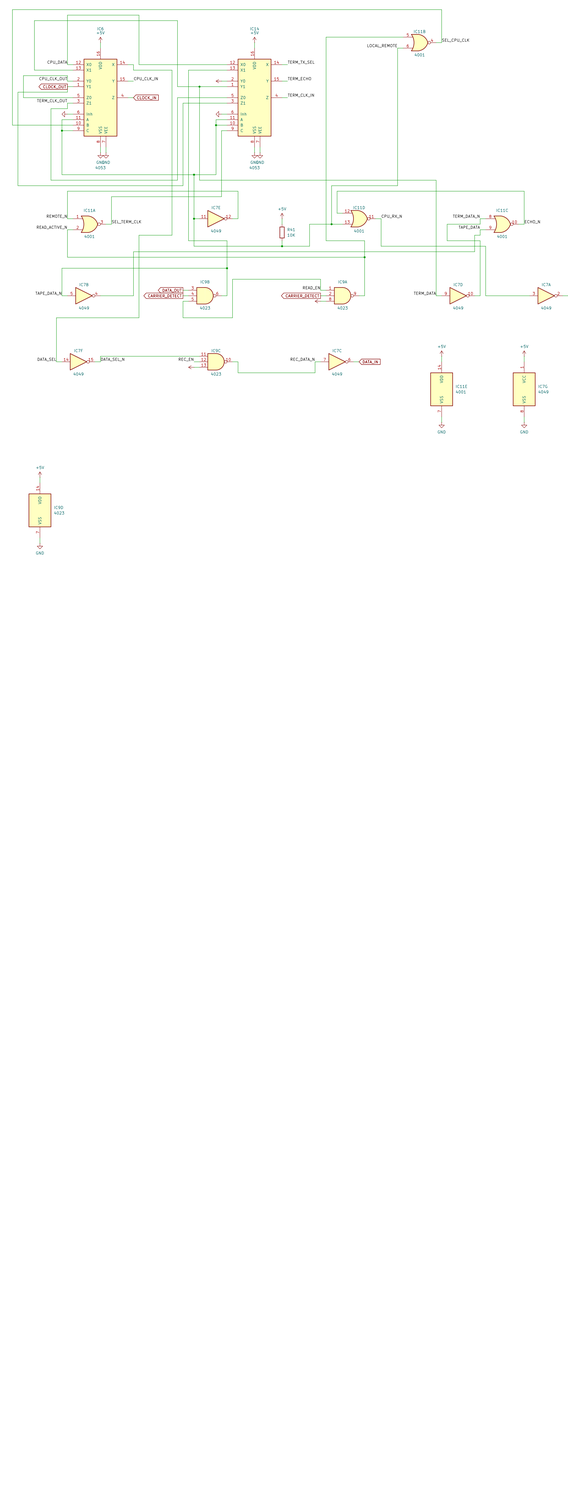Local/Remote steering and data/clock selectors




Record / read control latches and power-on reset


LED drivers, relay drivers, carrier-enable delay

Generated from docs/ac30_mod_demod.pdf (SWTPC AC-30 Cassette Tape Modulator/Demodulator
Schematic). Each block is wired; net labels join the blocks and sheets (identical labels are connected).
Transcription notes / assumptions:
- IC4 (4558) supply pins are not drawn. The assembly manual says IC4 runs from the +/-7.5 V
  zener rails (D12/D13 on the power supply sheet).
- R16's far end has a terminal dot with no label; taken as +5V (Q1/C8 timer pull-up).
- IC1B is unused and not drawn: its inputs are tied to GND, its outputs left open.
- The manual's text calls the pulse inverter IC2A; the schematic (followed here) uses IC2C.
Power input: the supply (sheet 3) is built as a separate unit; its six DC outputs come onto
the board on J12, a 6-pin KK-396 header (1 GND, 2 +5V, 3 +13V, 4 -13V, 5 +7.5V, 6 -7.5V). C23–C25 are +5 V bypass capacitors on the board
(drawn at the regulator on docs/ac30_PS.pdf; next to IC1, IC7 and IC13 on the original artwork).

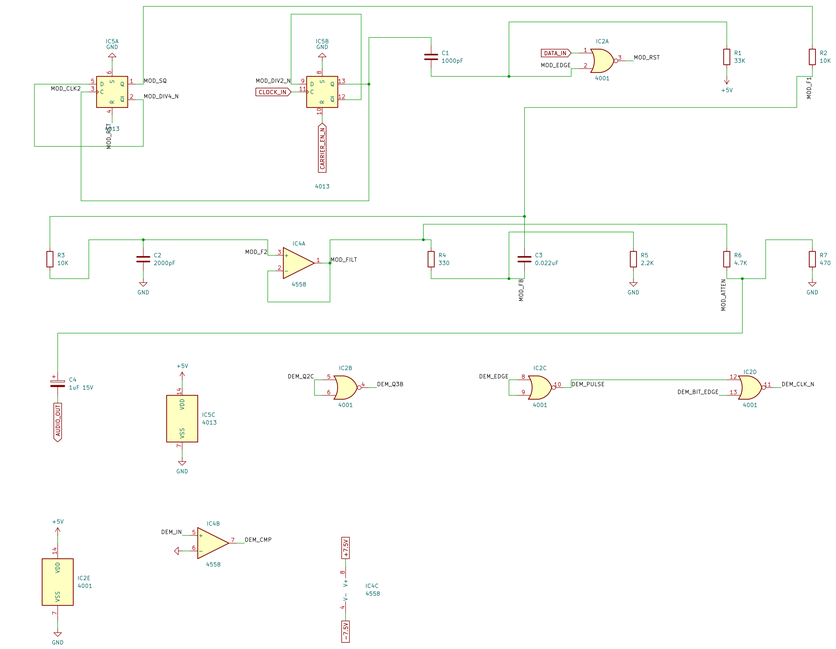Modulator: CLOCK IN /2 (IC5B), /1 or /2 by DATA IN (IC5A), 2-pole filter IC4A



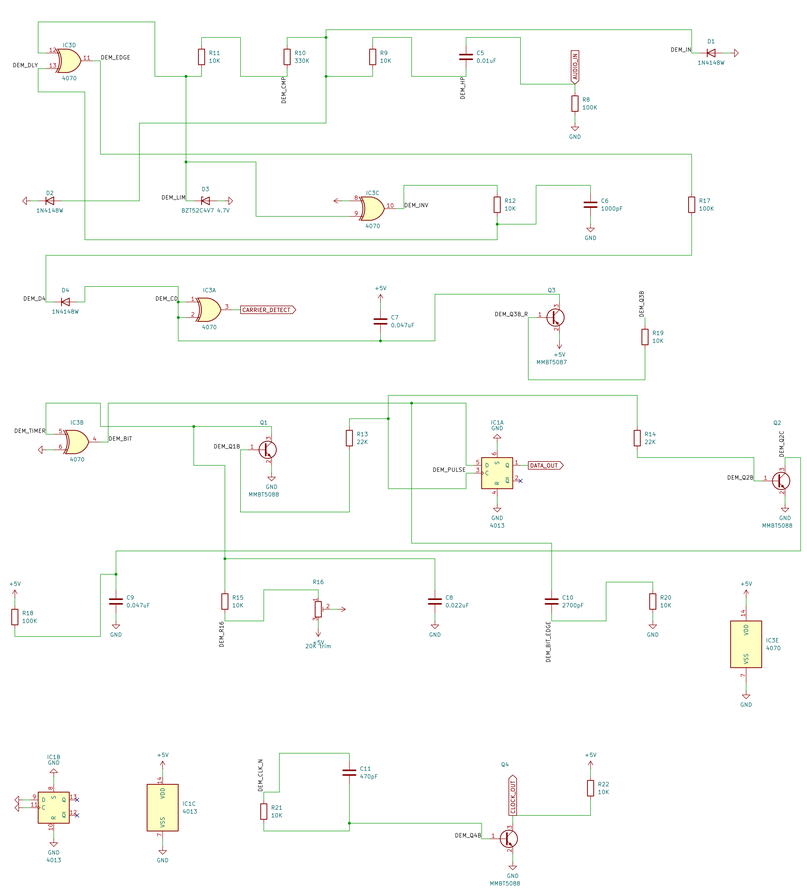Demodulator: comparator IC4B, edge pulses IC3C/D, carrier detect, data and 16X clock out



Power input connector (from the external supply) and +5 V bypass



Mounting holes



Generated from docs/ac30_PS.pdf (SWTPC AC-30 Audio Cassette Power Supply Schematic).
Built as an EXTERNAL unit: these parts have no footprints and are not on the PC board. Wire the six outputs to the board's power input J12 (KK-396: 1 GND, 2 +5V, 3 +13V, 4 -13V, 5 +7.5V, 6 -7.5V).
Transcription notes / corrections:
- The drawing joins the IC16 GND / C23-C25 return line to the bridge's negative corner (-13 V) through two crossings. That would put the 7805's ground at -13 V, so IC16 GND is taken as GND.
- T1's two 120 V primaries are drawn in parallel (120 VAC); drawn here as one primary. The 18 VAC secondary is centre-tapped, tap to GND: the bridge gives +13 V (C21) and -13 V (C22).
- D14-D17 numbering within the bridge is not shown on the drawing; assigned here.
- S6 is an SPDT toggle (BOM) used as an on/off switch; one throw is unused.
- IC15 (1488) supply pins are not drawn on the switching schematic; taken as +/-13 V, the only load for those outputs. IC4 (4558) uses +/-7.5 V (assembly manual).

PWR_FLAG
GND
PWR_FLAG
+13V
PWR_FLAG
-13V
PWR_FLAG
+7.5V
PWR_FLAG
-7.5V
PWR_FLAG
AC_LINE

Power supply (external): 120 VAC -> T1 -> bridge D14-D17 -> +/-13 V, zeners +/-7.5 V, 7805 +5 V

