Generated from docs/ac30_schematics.jpg (SWTPC AC-30 Cassette Tape Switching Schematic).
Split into 4 sheets: ac30_schematics.jpg, Each block is wired: net labels join the blocks and sheets (identical labels are connected).
Transcription notes / assumptions:
- 74LS00 pinout assumed (not explicitly called out in the real pinouts: IC70 drawn 8-->9 (VDD: 9-->10):
  - IC11C drawn inputs 9,10 (4070: 8,9).
  - 4053 NH (pin 6) and VEE (pin 7) are not shown on the drawing: tied to GND.
  - 4053 INH (pin 6) and VEE (pin 7) are not shown on the drawing.
  - IC15 (1488) supply pins are not shown: taken as +15V / -15V from the power supply (sheet 3).
  - CONTROL INVERT drawn as 4N2 pull-up: R is also brought out on J5.
  - J5 pin 10 (CARRIER DETECT) is driven by the cassette interface (sheet 2).
  - The front panel is wired to the rear of S1 in through-hole pads instead of the artwork's 22-pin connector and ribbon cable. SWITCHES: J1 pin 1 = MIC A, pin 2 = MIC B, pin 3 = RECORD A/B common, pin 4 = RELAY 1, pin 5 = RELAY 2, pin 6 = AUDIO_OUT, pin 7 = AUDIO_IN, pin 8 = READ/PLAY, pin 9 = REC/PLAY, pin 10 = LOCAL/REMOTE. MIC/EAR sockets: J2 = MIC A, J3 = MIC B, J4 = EAR A, J5 = EAR B.
  - Trimmer R39 (DELAY, next to IC10 on the artwork) is not on any schematic: it is listed.
  - Fuse F1 (1A) is not shown.
  - The artwork's J2 pins 11,12 (18 VAC A/B) are given: the power supply is external.
SMT variant (kicad-smt/MC30_SMT): every on-board part is surface mount except the Molex KK-396 connectors (J1, J5) and the 2-pin power header (J6). Footprints: SOIC-14 ICs, SOT-23 transistors (MMBT5088 for 2N3222, MMBT5087/5087, SOT-23 Darlington EA-5210 (2N 2149?), 6.3x7.7 mm aluminium C16, Bourns 3314G trimmer R18, 5206 LED DIP, RLY1/RLY2 as Omron G6K-2F-Y 5V DPDT (2 Form C) signal relays (Panasonic TQ2-5V substituted) instead of 6 V DIL reed relays; check the coil polarity mark (pin 1 to RELAY_x).


Mod/Demod & power input

File: AC30_SMT_modemod_power.kicad_sch

Power supply (external)

File: AC30_SMT_power_supply.kicad_sch


Front panel switches, LEDs and jacks

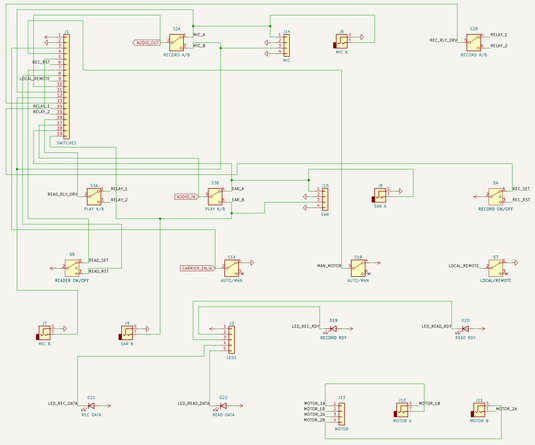


Board connectors (pin positions per original artwork)



RS-232 receivers / drivers, clock clamps

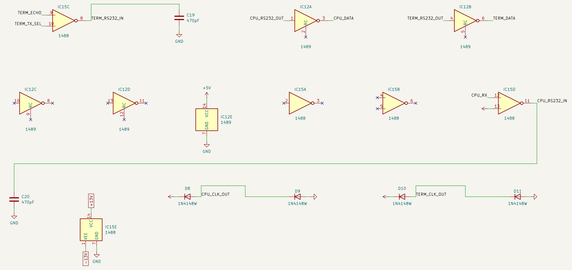

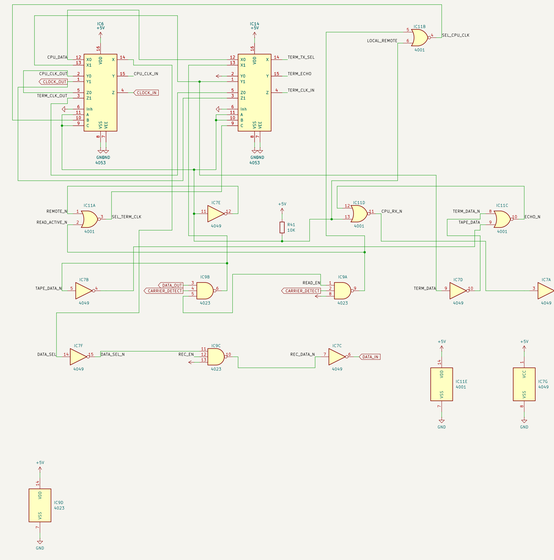Local/Remote steering and data/clock selectors




Record / read control latches and power-on reset

LED drivers, relay drivers, carrier-enable delay


Generated by kicad/tools/gen.py — edit netlist.py and regenerate, or edit in KiCad
Source: docs/ac30_schematics.jpg, docs/ac30_mod_demod.pdf, docs/ac30_PS.pdf, docs/AC30-BOM.m
SWTPC AC-30 reproduction
Sheet: /
File: AC_30_SMT.kicad_sch
Title: SWTPC AC-30 Cassette Interface — Switching (SMT)
Size: A3 | Date: 2026-05-08 | Rev: A
KiCad 8.0.4, 10.0.7 | ID: 1/3

Generated from docs/ac30_mod_demod.pdf (SWTPC AC-30 Cassette Tape Modulator/Demodulator
Schematic). Each block is wired; net labels join the blocks and sheets (identical labels are connected).
Transcription notes / assumptions:
- IC4 (4558) supply pins are not drawn. The assembly manual says IC4 runs from the +/-7.5 V
  zener rails (D12/D13 on the power supply sheet).
- R16's far end has a terminal dot with no label; taken as +5V (Q1/C8 timer pull-up).
- IC1B is unused and not drawn; its inputs are tied to GND, its outputs left open.
- The manual's text calls the pulse inverter IC2K; the schematic (followed here) uses IC2C.
Power input: the supply (sheet 5) is built as a separate unit; its six DC outputs come onto
the board on J12, a 6-pin RA-row header (1 GND, 2 +5V, 3 +13V, 4 +7.5V, 5 +7.5V, 6 -7.5V). C23–C25 are +5 V bypass capacitors on the board
(drawn at the regulator on docs/ac30_PS.pdf; next to IC1, IC7 and IC13 on the original artwork).

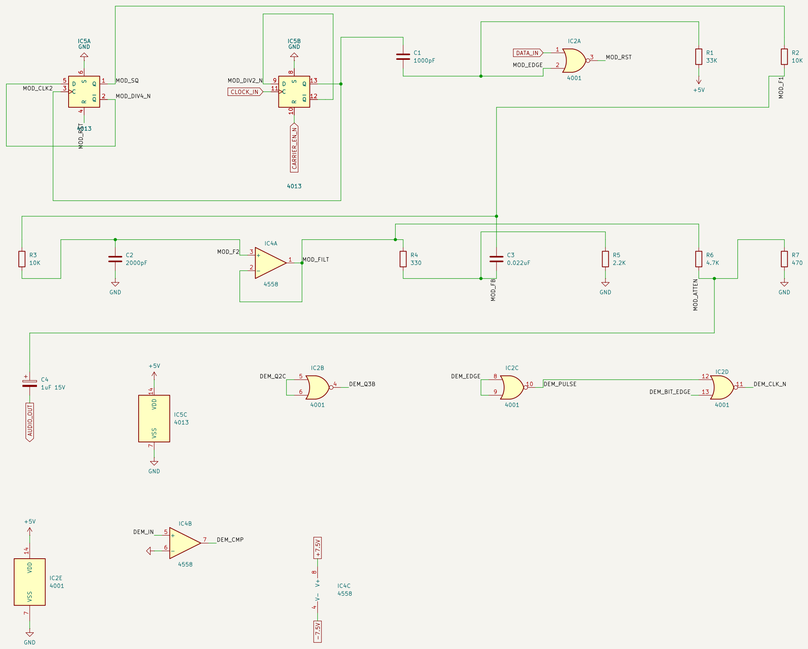
Modulator: CLOCK IN /2 (IC5B), /1 or /2 by DATA IN (IC5A), 2-pole filter IC4A



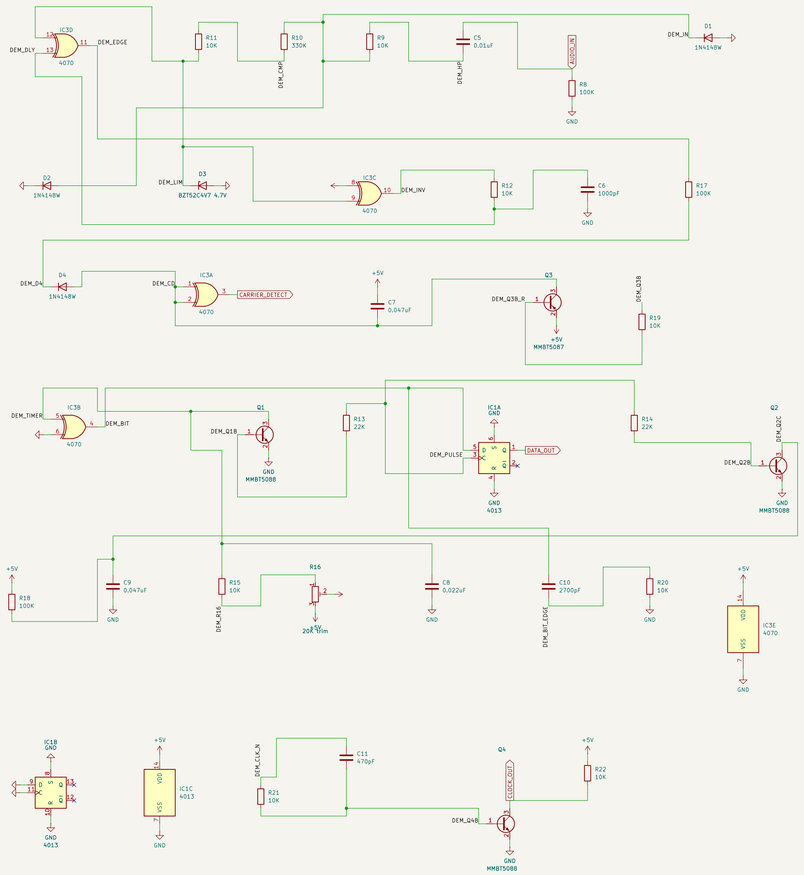
Demodulator: comparator IC4B, edge pulses IC3C/D, carrier detect, data and 16X clock out



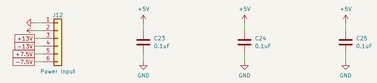Power input connector (from the external supply) and +5 V bypass



Mounting holes

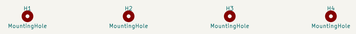

Source: docs/ac30_mod_demod.pdf; power input J12 for the external supply
SWTPC AC-30 reproduction
Sheet: /Mod/Demod & power input/
File: AC30_SMT_moddemod_power.kicad_sch


Title: SWTPC AC-30 — Modulator/Demodulator & power input

Size: A1	Date: 2026-10-08	**Rev: A**
KiCad E.D.A. 10.0.7		Id: 2/3

Generated from docs/ac30_PS.pdf (SWTPC AC-30 Audio Cassette Power Supply Schematic).
Built as an EXTERNAL unit: these parts have no footprints and are not on the PC board. Wire the six outputs to the board's power input J12 (KK-396: 1 GND, 2 +5V, 3 +13V, 4 -13V, 5 +7.5V, 6 -7.5V).
Transcription notes / corrections:
- The drawing joins the IC16 GND / C23-C25 return line to the bridge's negative corner (-13 V) through two crossings. That would put the 7805's ground at -13 V, so IC16 GND is taken as GND.
- T1's two 120 V primaries are drawn in parallel (120 VAC); drawn here as one primary. The 18 VAC secondary is centre-tapped, tap to GND: the bridge gives +13 V (C21) and -13 V (C22).
- D14-D17 numbering within the bridge is not shown on the drawing; assigned here.
- S6 is an SPDT toggle (BOM) used as an on/off switch; one throw is unused.
- IC15 (1488) supply pins are not drawn on the switching schematic; taken as +/-13 V, the only load for those outputs. IC4 (4558) uses +/-7.5 V (assembly manual).

PWR_FLAG
GND
PWR_FLAG
+13V
PWR_FLAG
-13V
PWR_FLAG
+7.5V
PWR_FLAG
-7.5V
PWR_FLAG
AC_LINE

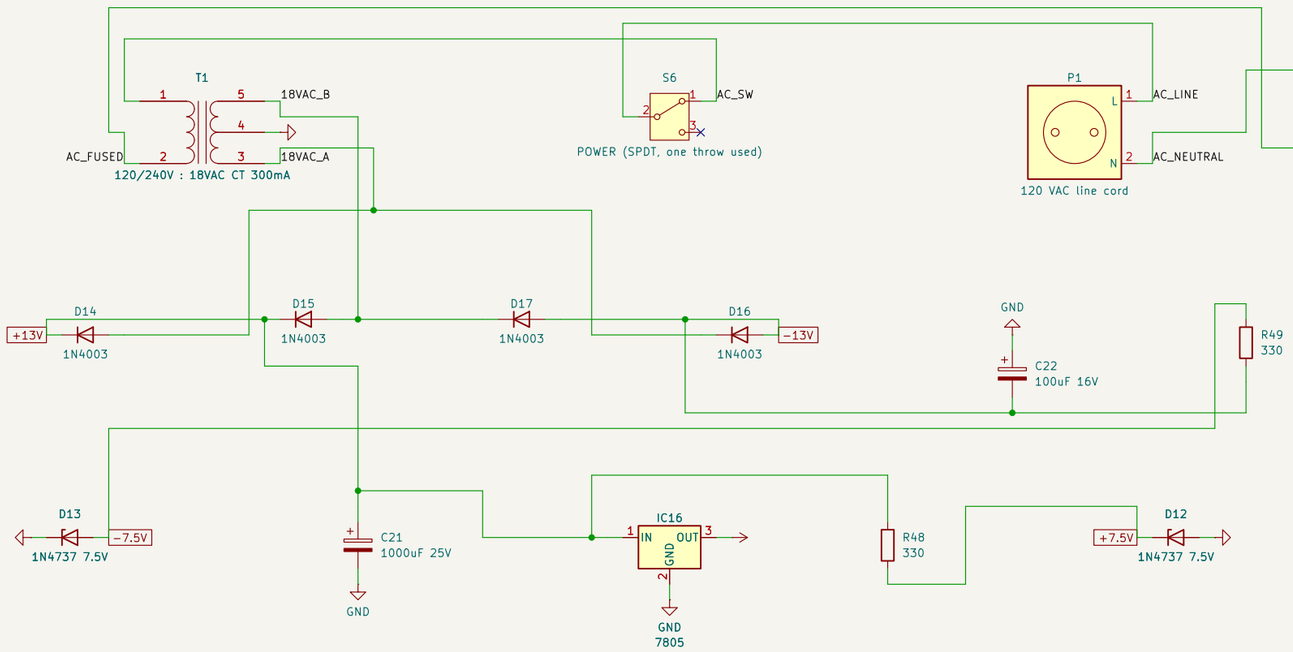Power supply (external): 120 VAC -> T1 -> bridge D14-D17 -> +/-13 V, zeners +/-7.5 V, 7805 +5 V



Source: docs/ac30_PS.pdf; parts have no footprints — built as a separate unit
SWTPC AC-30 reproduction
Sheet: /Power supply (external)/
File: AC30_SMT_power_supply.kicad_sch

Title: SWTPC AC-30 — Power supply (external, not on PCB)

Size: A3	Date: 2026-10-08	**Rev: A**
KiCad E.D.A. 10.0.7		Id: 3/3